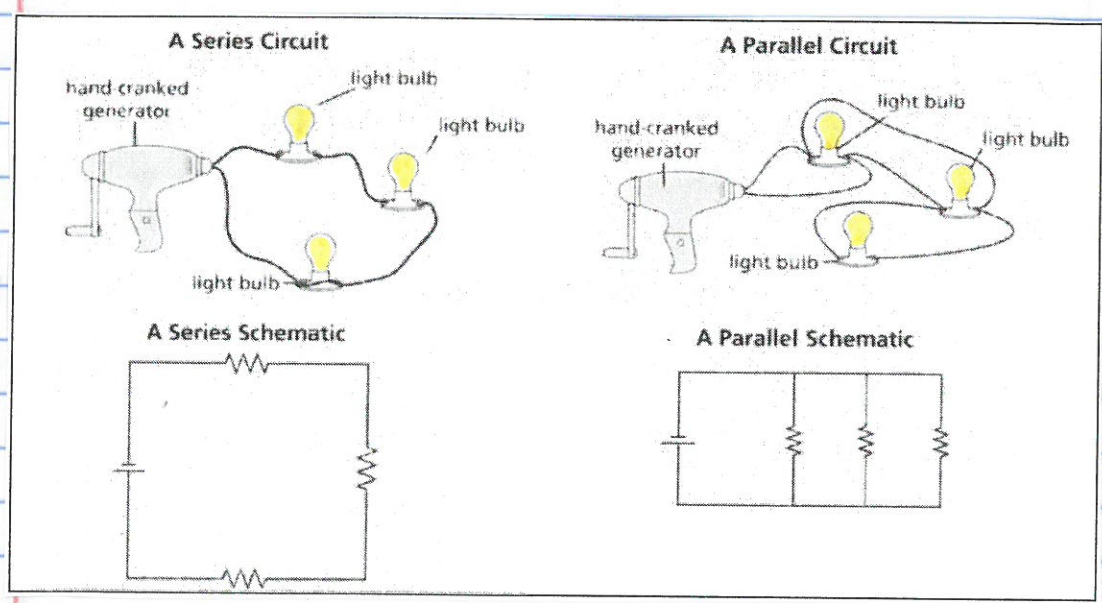


S3) Series and Parallel Circuits: Lighten Up
Investigate

Part B: Comparing Series and Parallel Circuits



2a.

2b.

Up

3a.

4a.

5a.

6a.